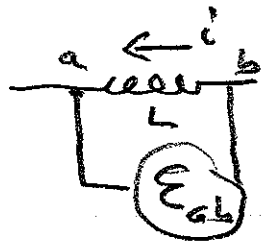


HW # 14 Solutions

30.10



$$\mathcal{E}_{ab} = +1.04 \text{ V}$$

$$\mathcal{E}_{ab} = -L \frac{dI}{dt}, \text{ therefore } \frac{dI}{dt} < 0 \text{ current decreasing}$$

$$\left| \frac{dI}{dt} \right| = \frac{|\mathcal{E}_{ab}|}{L} = \frac{1.04 \text{ V}}{0.260 \text{ H}} = 4 \text{ A/s}$$

$$I(2\text{s}) = 12 \text{ A} - (2 \text{ s})(4 \text{ A/s}) = 4 \text{ A}$$

30.11 for uniform B , $\Phi_B = BA$

$$B = \left(\mu_0 \frac{N}{\ell} I \right), \quad L = \frac{N \dot{\Phi}_B}{I} = \frac{\mu_0 N^2 a}{\ell}$$

30.20
$$I(t) = I_0 e^{-tR/L}$$

$$L = \frac{-tR}{\ln(I(t)/I_0)} = \frac{-2 \text{ ms}(15 \Omega)}{\ln\left(\frac{0.210 \text{ A}}{0.420 \text{ A}}\right)} = 93.3 \text{ mH}$$

30.32
$$\omega = 2\pi f = \frac{1}{\sqrt{LC}}$$

$$C = \frac{1}{4\pi^2 f_{\text{min}}^2 L} = \frac{1}{4\pi^2 (5.4 \times 10^5 \text{ Hz})^2 (2.37 \times 10^3 \text{ H})}$$

$$= 36.7 \text{ pF} \quad (1 \text{ pF} = 10^{-12} \text{ F})$$

30.40 a) $q(t) = A e^{-\frac{R}{2L}t} \cos(\omega' t + \phi)$

$$\dot{q} = -A \frac{R}{2L} e^{-\frac{R}{2L}t} \cos(\omega' t + \phi) - \omega' A e^{-\frac{R}{2L}t} \sin(\omega' t + \phi)$$

$$\ddot{q} = A \left(\frac{R}{2L} \right)^2 e^{-\frac{R}{2L}t} \cos(\omega' t + \phi) + 2\omega' A \left(\frac{R}{2L} \right) e^{-\frac{R}{2L}t} \sin(\omega' t + \phi) - \omega'^2 A e^{-\frac{R}{2L}t} \cos(\omega' t + \phi)$$

$$\ddot{q} + \frac{R}{L} \dot{q} + \frac{q}{LC} = q \left[\left(\frac{R}{2L} \right)^2 - \omega'^2 - \frac{R^2}{2L^2} + \frac{1}{LC} \right] = 0$$


$$\text{so } \omega' = \left[\frac{1}{LC} - \frac{R^2}{4L^2} \right]^{1/2}$$

b) At $t=0$, $q = Q$ & $\dot{q} = -\dot{q} = 0$

so $A \cos \phi = Q$ and $\dot{q}(0) = -\frac{R}{2L} A \cos \phi - \omega' A \sin \phi = 0$

giving $A = \frac{Q}{\cos \phi}$; $\tan \phi = -\frac{R}{2L\omega'}$

30.48 (a)

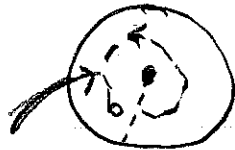


Amperean loop

inner conductor radius a

I out of page on inner

I into page on outer
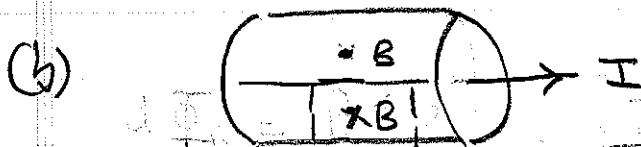
$$(a) \oint \vec{B} \cdot d\vec{\ell} = \mu_0 I \Rightarrow B(r) = \begin{cases} \frac{\mu_0 I}{2\pi r} & r < B \\ 0 & r > B \end{cases}$$



$$da = l dr$$

$$d\Phi_B = B(r) da = \frac{\mu_0 I l}{2\pi} \frac{dr}{r}$$

(c) Integrating,

$$\Phi_B = \int_a^b \frac{\mu_0 I r}{2\pi r} dr = \frac{\mu_0 I l}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$(a) L = \frac{\Phi_B}{I} = l \frac{\mu_0}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$(c) U_B = \frac{1}{2} L I^2 = \frac{l I^2 \mu_0}{4\pi} \ln\left(\frac{b}{a}\right)$$

$$30.57 \quad V_C = 12V; U_C = \frac{1}{2} C V_C^2$$

$$C = 2U_C / V_C^2 = 2(0.0160J) / (12V)^2 = 222 \mu F$$

$$f = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L = \left(\frac{1}{2\pi f}\right)^2 C = 9.31 \mu F$$

$f = 3500 \text{ Hz}$

30.59 magnetic field energy density, $u_B = B^2 / 2\mu_0$

$$u_B = 6.366 \times 10^4 \text{ J/m}^3$$

total magnetic energy in volume V , $U_B = V u_B$.


mass of material in sunspot $m = \rho V$, setting $K = U_B$:

$$\frac{1}{2}(\rho V) v^2 = V u_B \Rightarrow v = \sqrt{\frac{2 u_B}{\rho}} = 2 \times 10^4 \text{ m/s}$$

about $\frac{1}{30}$ the escape velocity from the surface of the sun.

HW 14

-4-

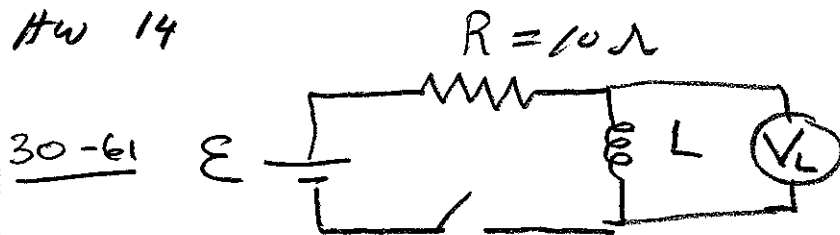

switch closed @ $t=0$

- a) Voltage across R increases with time, whereas voltage across L decreases with time as in the graph
- b) Since $V_L(t) \xrightarrow{t \rightarrow \infty} \text{constant} \approx 15V$, inductor has some internal resistance (R_L).

c) At $t=0$, $I(0) = 0$ so $\mathcal{E} = V_L(t) = 50V$ from graph

d) From graph, $V_L(t) \xrightarrow{t \rightarrow \infty} I_{\max} R_L = 15V$
 $\mathcal{E} - I_{\max} (R + R_L) = 0$; $I_{\max} = \frac{50V - 15V}{10\Omega} = 3.5A$

e) $R_L = \frac{15V}{3.5A} = 4.3\Omega$; $R_{TOT} \equiv R_L + R$
 $\tau \equiv L / R_{TOT}$

We can get L from τ .

$$I(t) = \frac{\mathcal{E}}{R_{TOT}} (1 - e^{-t/\tau})$$


$$V_L(t) = \mathcal{E} - IR = \mathcal{E} \left[1 - \frac{R}{R_{TOT}} (1 - e^{-t/\tau}) \right]$$

$$\text{When } t = \tau, V_L(\tau) = 50V \left[1 - \frac{10}{14.3} (1 - \frac{1}{e}) \right] = 27.9V$$

From the graph, $\tau \approx 3 \text{ ms}$, $L = 14.3\Omega (3 \text{ ms}) = \underline{43 \text{ mH}}$

30-64.

$$25V = \mathcal{E}$$

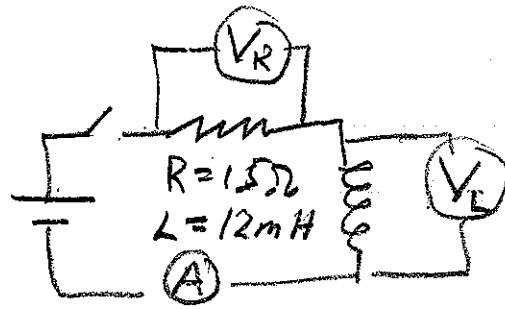

switch closed @
 $t = 0$.

L has negligible internal
resistance

a) At $t = 0$, $I = 0$, $V_R = 0$, $V_L = \mathcal{E} = 25V$

b) For $t \gg L/R$ $I = I_{max} = \frac{\mathcal{E}}{R} = 1.67A$
 $V_R = 25V$, $V_L = 0$

c) None of these answers depend on L .