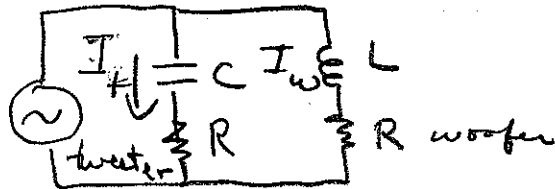


HW #15 Solutions31.40


$$a) Z_T = R + \frac{1}{i\omega C}; |Z_T| = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} \quad \text{tweeter}$$

$$b) Z_w = R + i\omega L; |Z_w| = \sqrt{R^2 + (\omega L)^2} \quad \text{woofer}$$

$$c) \text{ if } Z_T = Z_w, I_T = I_w$$

$$d) \text{ at the crossover point } (Z_T = Z_w)$$

$$\omega = \frac{1}{\sqrt{LC}}; f = \frac{1}{2\pi\sqrt{LC}}$$

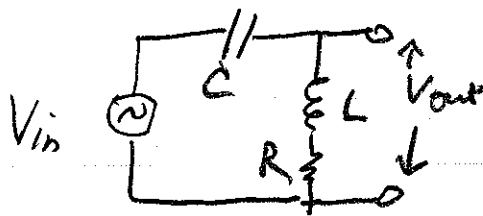31.49 High-pass filter

$$\frac{V_{out}}{V_{in}} = \frac{R + i\omega L}{\frac{1}{i\omega C} + R + i\omega L} = g e^{i\phi}$$


$$|g(\omega)|^2 = \frac{(R + i\omega L)(R - i\omega L)}{R + i(\omega L - \frac{1}{\omega C})} \left(\frac{R - i\omega L}{R - i(\omega L - \frac{1}{\omega C})} \right)$$

$$g(\omega) = \sqrt{\frac{R^2 + (\omega L)^2}{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad \begin{matrix} \xrightarrow{\omega \rightarrow \infty} \\ \omega \rightarrow 0 \end{matrix} \quad \begin{matrix} \omega C \\ \omega \rightarrow 0 \end{matrix}$$

$$g(\omega) \xrightarrow{\omega \rightarrow \infty} \frac{\omega L}{\omega L} = 1$$

HW 15

31.50

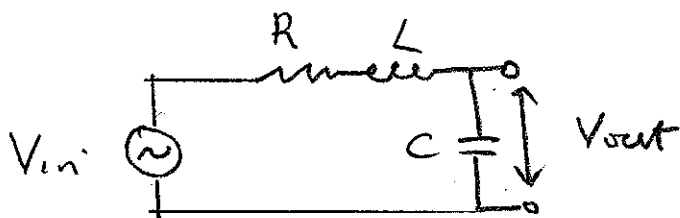

$$\frac{V_{out}}{V_{in}} = \frac{1/i\omega C}{R + i(\omega L - 1/\omega C)} = g e^{i\phi}$$

$$g(\omega) = \frac{1/\omega C}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} \xrightarrow{\omega \rightarrow 0} \frac{1/\omega C}{1/\omega C} = 1$$

$$g(\omega) \xrightarrow{\omega \rightarrow \infty} \left(\frac{1}{\omega C}\right) \left(\frac{1}{\omega C}\right) \rightarrow 0$$

31.53 In L-R-C circuit, $I(t) = I(\omega) e^{i\omega t}$

$$I(\omega) = \frac{E_0}{R + i(\omega L - 1/\omega C)} = |I(\omega)| e^{i\phi}$$

Voltage across capacitor is:

$$V_C(\omega) = \frac{1}{i\omega C} I(\omega) = |V_C(\omega)| e^{i\phi_C}$$

$$V_C(t) = |V_C(\omega)| \cos(\omega t + \phi_C)$$

$$I(t) = |I(\omega)| \cos(\omega t + \phi)$$

since $\langle \cos(\omega t + \theta) \rangle_T = \frac{1}{2}$

$$U_E = \frac{1}{4} C |V_C(\omega)|^2 ; U_B = \frac{1}{4} L |I(\omega)|^2$$

Calculating the modulus of $I(\omega)$:


$$|I(\omega)| = \frac{\mathcal{E}_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

and $|V_C(\omega)| = \left| \frac{1}{i\omega C} I(\omega) \right| = \frac{1}{\omega C} |I(\omega)|$


So $U_E = \frac{1}{4} \frac{1}{\omega^2 C} |I(\omega)|^2$

$$U_B = \frac{L}{4} |I(\omega)|^2$$

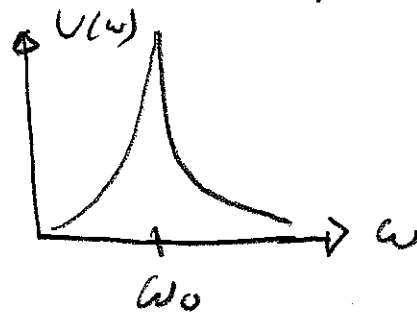Both $U_E(\omega)$, $U_B(\omega)$ go to zero at $\omega=0$ and at $\omega \rightarrow \infty$. They both peak at $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$



31.54

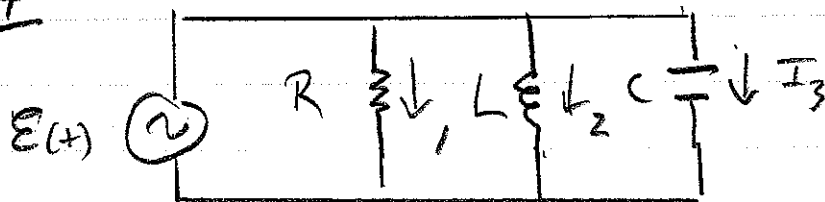

$$I_1 = \mathcal{E}_0 / R$$

$$I_2 = \mathcal{E}_0 / i\omega L$$

$$I_3 = \mathcal{E}_0 i\omega C$$

$$I = I_1 + I_2 + I_3$$

$$= \mathcal{E}_0 \left(\frac{1}{R} + \frac{1}{i\omega L} + i\omega C \right)$$

$$|Z|^{-1} = \left[\frac{1}{R^2} + (\omega C - \frac{1}{\omega L})^2 \right]^{-1/2}$$

magnitude of current is,

$$|I(\omega)| = \varepsilon_0 \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{\omega L} - \omega C\right)^2}$$

$$= \sqrt{|I_1|^2 + (|I_2| - |I_3|)^2}$$

31.64 a) $\omega_0 = \frac{1}{\sqrt{LC}} \Big| = 786 \text{ rad/s}$
 $L = 1.84$
 $C = 0.9 \mu\text{F}$

b) $|Z(\omega_0)|^2 = \sqrt{R^2 + (\omega_0 L - 1/\omega_0 C)^2} = R = 300 \Omega$

$I_{\text{rms}}(\omega) = \frac{V_{\text{rms}}}{Z(\omega)} \Big|_{\omega = \omega_0} = 0.200 \text{ A}$

c) $\frac{1}{2} I_{\text{rms}}(\omega) = \frac{1}{2} \frac{V_{\text{rms}}}{|Z(\omega_0)|} \Rightarrow \frac{1}{|Z(\omega)|} = \frac{1}{2R}$

$|Z(\omega)|^2 = 4R^2 = R^2 + (\omega L - 1/\omega C)^2$

$(\omega^2 LC - 1)^2 = 3\omega^2 R^2 C^2$

$\omega^4 (LC)^2 - \omega^2 (3R^2 C^2 - 2LC) + 1 = 0$

$\omega^4 - \omega^2 \frac{3R^2 C^2 - 2LC}{(LC)^2} + \left(\frac{1}{LC}\right)^2 = 0$

hw #15

-5-

Solving quadratic and putting in the values.

$$\omega_{\pm}^2 = \begin{cases} 8.90 \times 10^5 \text{ (rad/s)}^2 \\ 4.28 \times 10^5 \text{ (rad/s)}^2 \end{cases}$$

$$\omega_{+} = 943 \text{ rad/s}; \quad \omega_{-} = 654 \text{ rad/s}$$

(d)

<u>R</u>	<u> I(\omega_0) </u>	<u>$\omega_{+} - \omega_{-}$</u>
300 Ω	0.200 A	289 rad/s
30 Ω	2 A	28.9 rad/s
3 Ω	20 A	2.89 rad/s